


## LOGICAL OPERATIONS

### • OR GATE

A	B	y
0	0	0
1	0	1
0	1	1
1	1	1

Binary levels from voltage

1 → 4-5V (say)  
0 → 0-1V

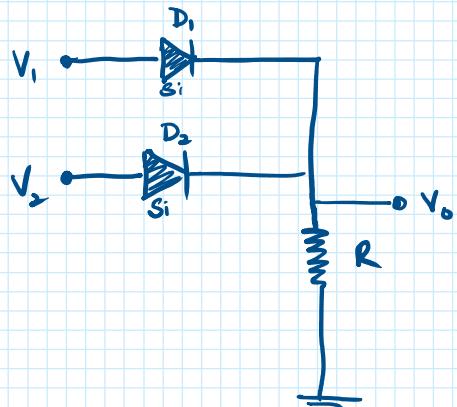


V <sub>1</sub>	V <sub>2</sub>	V <sub>0</sub>
0V [0]	0V [0]	0V [0]
0V [0]	5V [1]	4.3V [0]
5V [1]	0V [0]	4.3V [1]
5V [1]	5V [1]	4.3V [2]

■ equivalent logic levels

### • AND GATE

A	B	y
0	0	0
0	1	0
1	0	0
1	1	1

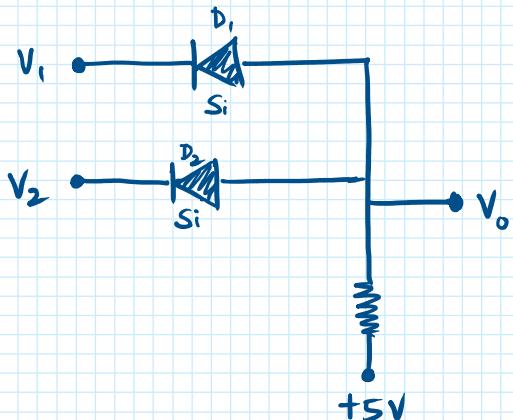

V <sub>1</sub>	V <sub>2</sub>	V <sub>0</sub>
0V [0]	0V [0]	0.7V [0]
0V [0]	5V [1]	0.7V [0]
5V [1]	0V [0]	0.7V [0]
5V [1]	5V [1]	5V [1]

EDA tools :  
to check analysis  
of circuits  
LTspice



## TRANSISTORS

"transfer + resistance"

Transfer of current from a low resistance region to a high resistance region
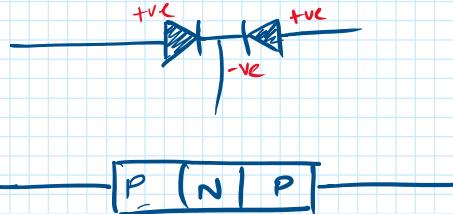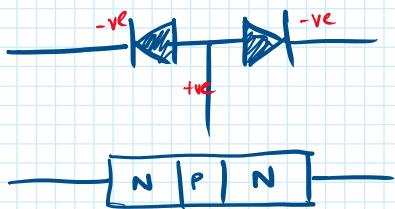
## ① BIPOLAR JUNCTION TRANSISTOR (BJT)





- Three terminal devices
- Constructed by connecting two p-n junctions back to back



- p-type/n-type sandwiched between two of its opposite types
- Bipolar ~~why~~ both majority and minority carrier actively participate in its operation

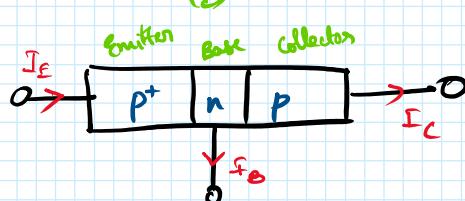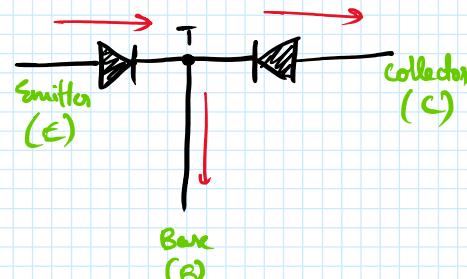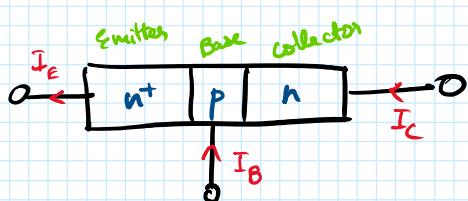
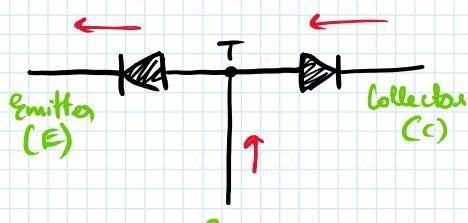
### Terminals

Three terminals : Emitter, base, collector



### NOTE

$p^+, n^+$  → more doped

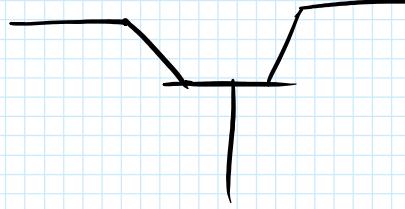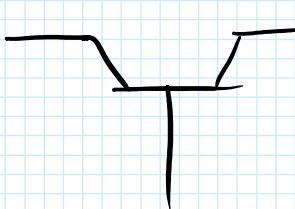

### EMITTER (E)

- supplies charge carriers
- heavily doped
- moderate in size

### BASE (B)

- middle portion; forms two p-n junctions b/w E, C
- lightly doped
- smallest in width
- controls no. of charge carriers emitted

### COLLECTOR (C)

- collects charge carriers
- moderately doped
- widest of all regions; maximum heat dissipated here

### TRANSISTOR BIASING

- Transistor has two p-n junctions:

## TRANSISTOR BIASING

- Transistor has two p-n junctions:
  - Emitter - base (EB)
  - Collector - base (CB)
- Each of these can be biased independently


Thus we have the following regions of operation:

	EB junction	CB junction	Application
Active region (common)	Forward	Reverse	works as amplifier
Saturation region	Forward	Forward	DN - switch (digital)
Cut-off region	Reverse	Reverse	OFF - switch (digital)
Inverse active region (rare)	Reverse	Forward	Attenuator

## ACTIVE REGION

- Emitter current =  $I_E = I_C + I_B$
- Collector current =  $I_C = I_{C(\text{majority})} + I_{C(\text{minority})}$

## CB INPUT CHARACTERISTIC CURVE

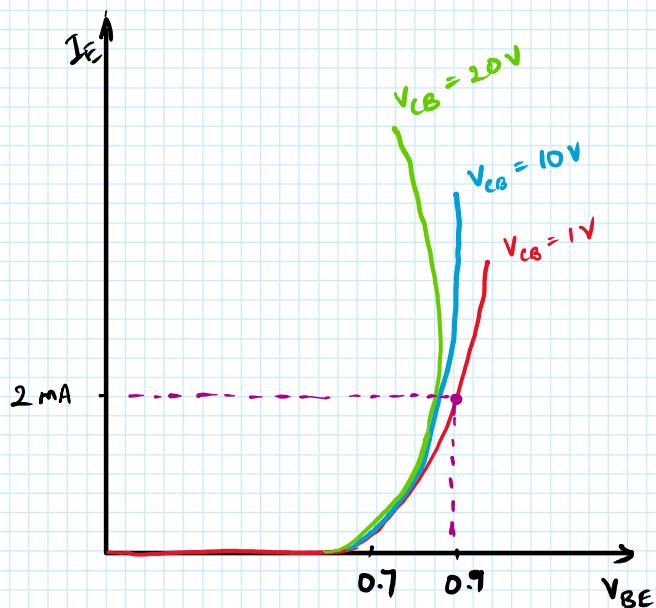

## EARLY EFFECT / BASE WIDTH MODULATION

Curve shifting towards the left or inwards  $\rightarrow$  "Early Effect" [or]  
Base Width Modulation

NOTE: Base width  
[fill]

$$\text{Input impedance (resistance)} = \frac{\Delta V_{BE}}{\Delta I_E}$$

Using pt. from graph,

Using  $\text{ht}$  from graph,

$$g_i = \frac{0.9 - 0.6}{2\text{mA} - 0.5\text{mA}} = \frac{0.3}{1.5\text{mA}}$$

$$g_i = 200 \Omega$$

Thus,  $g_i$  value is less.

$$\begin{aligned} I_c &= I_{c_{\text{majority}}} + I_{c_{\text{minority}}} \\ &= \alpha I_E + I_s \end{aligned}$$

$$I_c = \alpha I_E + I_{c_{\text{BO}}} \quad \begin{array}{l} \text{current from collector to base} \\ \text{denotes that emitter terminal is Open} \end{array}$$

$$\boxed{I_c = \alpha I_E}$$

$$\left. \alpha = \frac{I_c}{I_E} \right\} \text{Current gain / Current amplification factor}$$

$$\alpha \rightarrow 0.9 \text{ to } 0.99; \text{ ideally assume } \alpha = 1$$

Hence in ideal case,

$$\boxed{I_c \approx I_E}$$

$\therefore$  BJT is a current controlled device in active region.

## NUMERICALS

Q: In a CB connection, current amplification factor is 0.9,  $I_E = 1\text{mA}$ . Find base current.

Soln:  $\alpha = \frac{I_c}{I_E}$

$$\begin{aligned} I_c &= (1\text{mA})(0.9) \\ &= 0.9\text{ mA} \end{aligned}$$

$$I_E = I_c + I_B$$

$$\begin{aligned} I_B &= I_E - I_c = 1\text{mA} - 0.9\text{mA} \\ &= 0.1\text{mA} \end{aligned}$$

$$\begin{aligned}
 I_B &= I_E - I_C = 1\text{mA} - 0.9\text{mA} \\
 &= \underline{\underline{0.1\text{mA}}} \\
 &\quad [\text{Or}] \\
 &= \underline{\underline{100\mu\text{A}}}
 \end{aligned}$$

Q:  $I_C = 0.95\text{mA}$

$I_B = 0.05\text{mA}$

$\alpha = ?$

Soh:  $I_E = I_C + I_B$

$I_E = 1\text{mA}$


$$\alpha = \frac{I_C}{I_E} = \frac{0.95}{1} = \underline{\underline{0.95}} \quad \boxed{\text{no units}}$$

Q: In CB connection,  $I_E = 1\text{mA}$ ,  $\alpha = 0.92$ . If emitter circuit is open, the collector current  $I_{CBO} = 50\mu\text{A}$ . Find total  $I_C$ .

Soh:  $I_C = \alpha I_E + I_{CBO}$

$$\begin{aligned}
 &= 0.92(1 \times 10^{-3}) + (50 \times 10^{-6}) \\
 &= 9.7 \times 10^{-4} \\
 &= \underline{\underline{0.97\text{mA}}}
 \end{aligned}$$
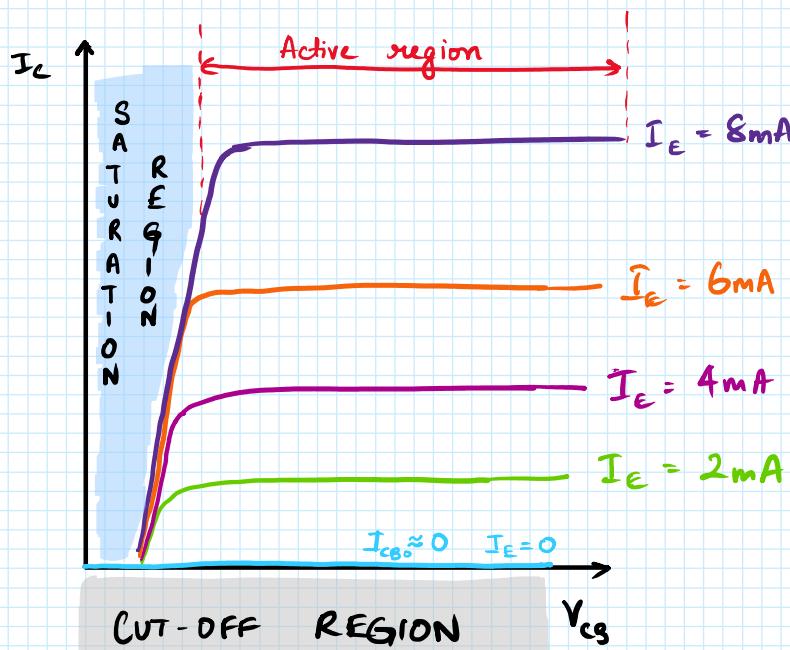
### CB OUTPUT OR COLLECTOR CHARACTERISTICS



$$r_{\text{L}} = \frac{\Delta V_{\text{CB}}}{\Delta I_{\text{C}}} = \frac{15 - 5}{(6 - 6) \text{ mA}} = \infty ] \text{ infinity as we have taken } \alpha = 1$$

$r_{\text{L}}$   $\rightarrow$  output impedance  $\rightarrow$  very high