

Types of Diode Breakdown, Diode Approximations

13 September 2023 10:50

TYPES OF DIODE BREAKDOWN

Avalanche breakdown

Under reverse bias,

Voltage increases → Depletion region widens → Accumulation of more immobile ions


Collision with ←
other atomic
structures

Kinetic energy ←
is provided
to charge carriers

Electric field
is generated

↓
Releases more
charge carriers;
covalent bonds broken,
electron-hole generating

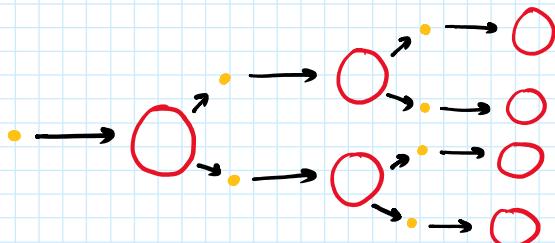- Happens due to impact ionisation / avalanche multiplication




- Motion of these charge carriers creates a sudden jump in current, often damaging the diode itself

Zener Breakdown

- Occurs in Zener diode → Both p and n heavily doped
- Due to more charge carriers, depletion region is narrower in normal state
- Smaller reverse bias voltage → stronger electric field

↓
more charge carriers
liberated

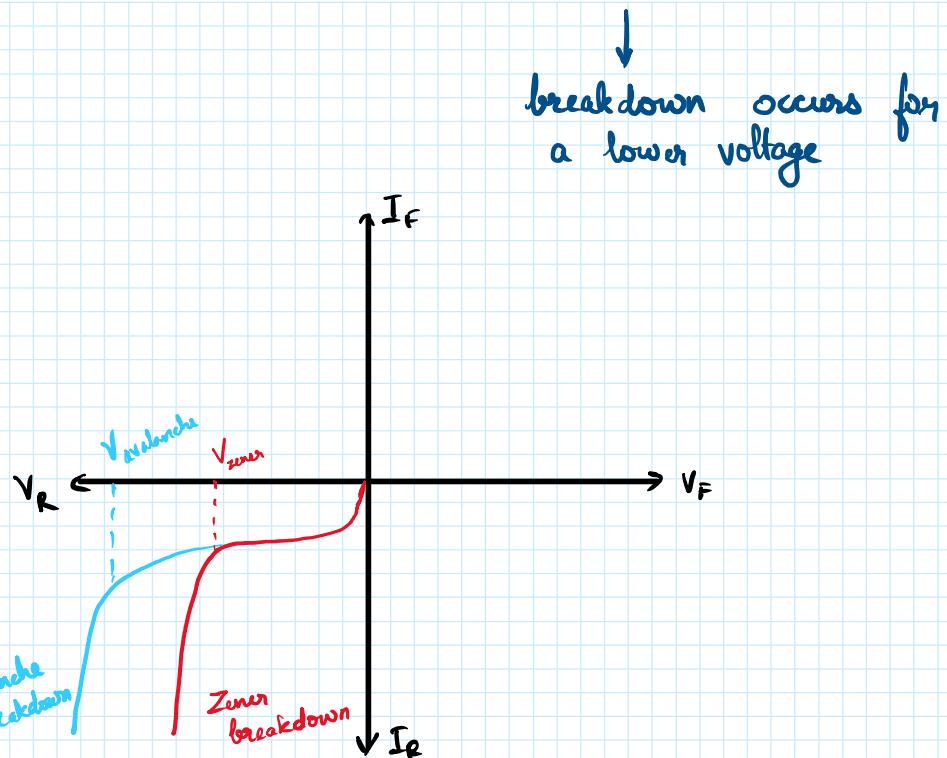

DIODE APPROXIMATIONS / EQUIVALENT DIAGRAMS

Mathematical method to approximate non-linear behaviour of real diodes

three types

First Approximation (Ideal Diode Characteristics)

Second Approximation (Simplified Diode Characteristics)


Third Approximation (Linear Piece-wise Diode Characteristics)

First Approximation (Ideal Diode Characteristics)

FORWARD BIAS: Closed switch, no voltage drop



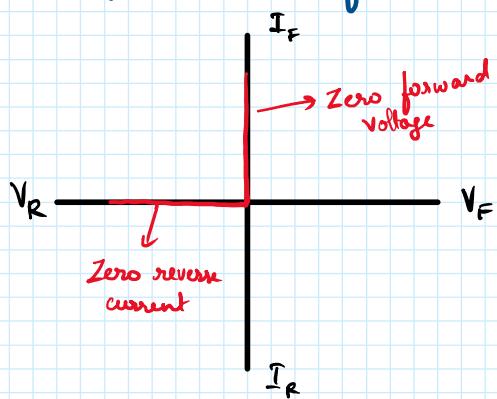
REVERSE BIAS: Open switch, infinite resistance



Second Approximation (Simplified Diode Characteristics)


Second Approximation (Simplified Diode Characteristics)

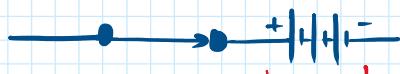FORWARD BIAS: In series with a battery to turn on, specific knee voltage is given



→ 0.7 V or greater for Si

REVERSE BIAS: Open switch

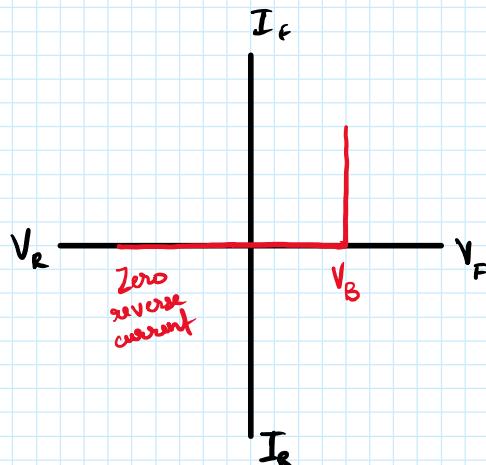


Third Approximation (Linear Piece-wise Diode Characteristics)

FORWARD: Includes knee voltage as well as voltage across bulk resistance R_B


Voltage drop V_D

$$V_D = 0.7 \text{ V} + (I_D)(R_B)$$

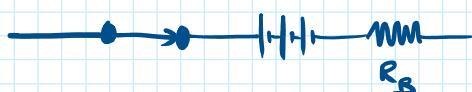Annotations: "knee voltage" points to 0.7 V, "bulk resistance" points to R_B , and "voltage across bulk resistance" points to the term $(I_D)(R_B)$.




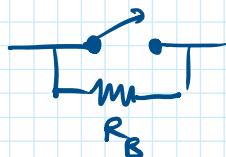REVERSE: Open switch with R_B in parallel




I_f



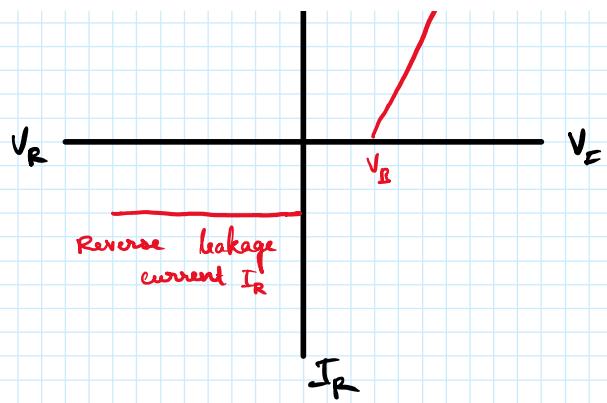

PROBLEMS

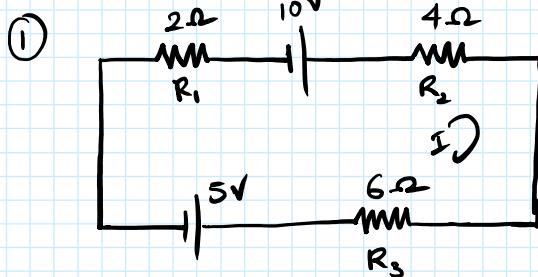

Sohu: Using KVL,

→ REVISE

$$10 - 4I - 6I - 5 - 2I = 0$$



$$5 - 12I$$


② A Si diode and Ge diode are connected in series with a $2k\Omega$ resistor. If each diode has an internal resistance of 5Ω , find the diode current for both piece-wise linear circuit and simplified circuit if applied voltage is

(a) $V_D = 1V$

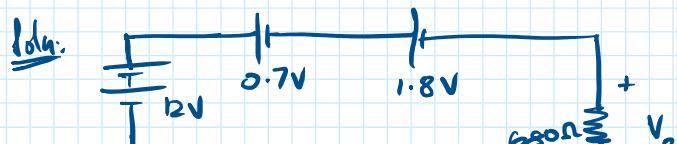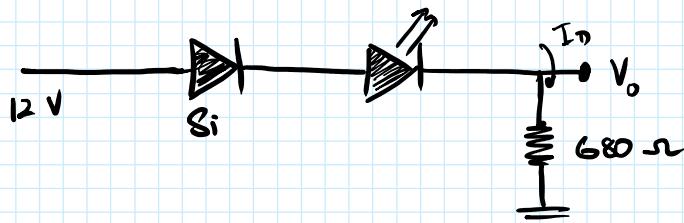(b) $V = 5V$

③ Determine V_o , I_D for given series diode circuit. Assume LED voltage as $1.8V$



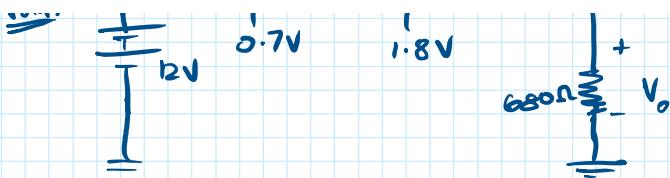



$$V_o = 12 - 0.7 - 1.8 \\ = \underline{\underline{9.5 \text{ V}}}$$

$$9.5 - 680 I_D = 0$$

$$I_D = \frac{-9.5}{-680}$$

$$= \underline{\underline{0.013 \text{ A}}}$$

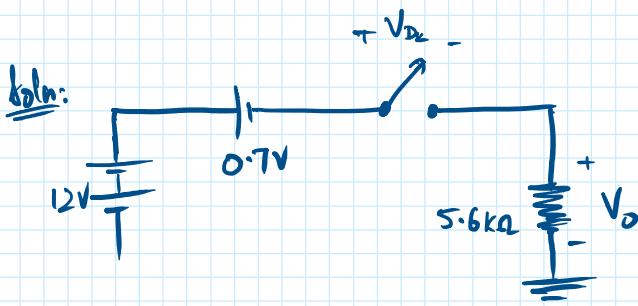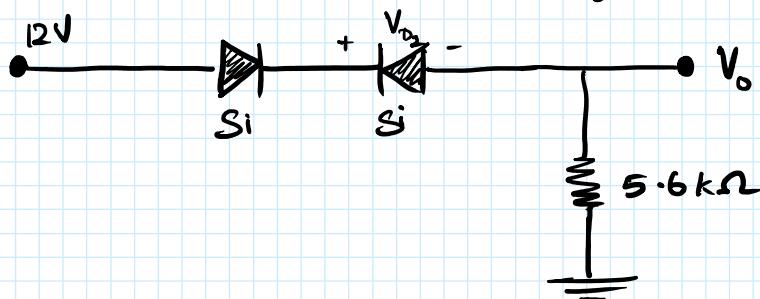④ Determine I_D , V_{D_2} & V_o for given circuit




$$I_D = 0$$



$$V_o = 5.6 \text{ k}\Omega \times I_D$$

$$V_o = 0$$

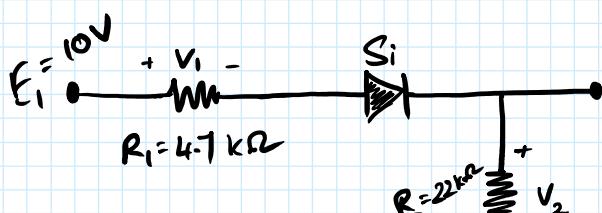⑤ Determine V_1 , V_2 , V_o , I in the given circuit



$$R_1 = 4.7 \text{ k}\Omega$$

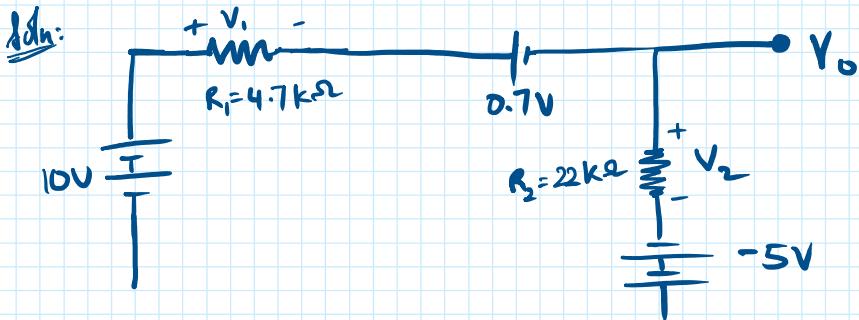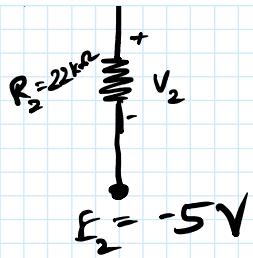

Using KVL,

$$10 - 4.7kI - 0.7 - 22kI + 5 = 0$$

$$14.3 - 26.7kI = 0$$

$$I = \frac{-14.3}{-26.7 \times 10^3} = 5.35 \times 10^{-4} \text{ A}$$

$$V_1 = IR_1$$

$$= 5.35 \times 10^{-4} \times 4.7 \times 10^3$$


$$= 2.51 \text{ V}$$


$$V_2 = IR_2$$

$$= 5.35 \times 10^{-4} \times 22 \times 10^3$$

$$= 11.77 \text{ V}$$

$$-5 + V_2 - V_o = 0$$

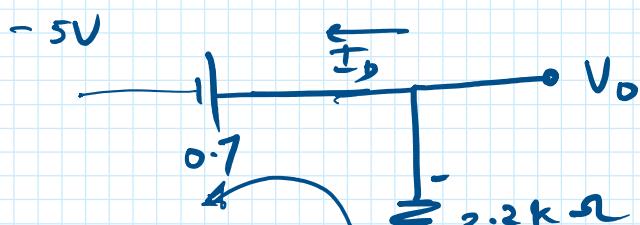

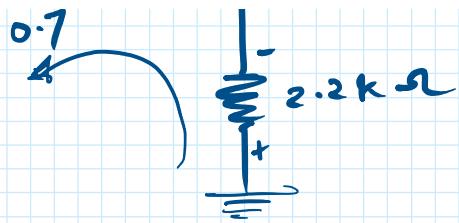

$$-2.2kI - 0.7 + 5 = 0$$

$$I = \frac{-4.3}{-2.2 \times 10^3} = 1.95 \times 10^3 A$$

~~A~~

$$V_o = I(2.2k)$$

$$= \underline{\underline{4.3 V}}$$