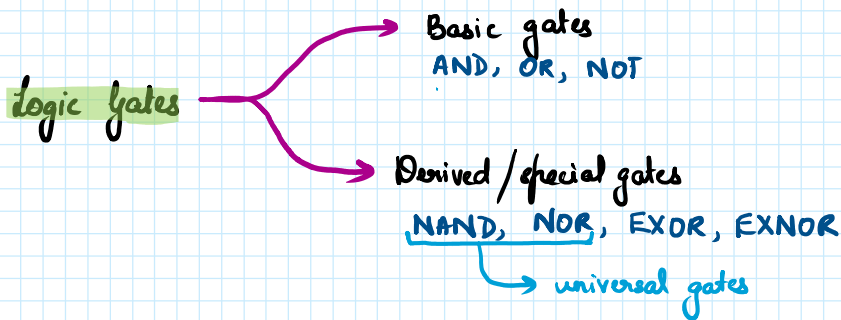


# 1. Boolean Algebra & Logic Gates

07 November 2023 09:39

## BOOLEAN ALGEBRA, LOGIC GATES - INTRO


- Mathematics used to analyse and simplify logic/digital circuits  $\rightarrow$  boolean algebra
- Digital circuits  $\rightarrow$  constructed using logic gates
- Logic gates: one or more inputs, only one output
- Number of possible input states  $= 2^n \rightarrow$  no. of inputs



## AND GATE

All inputs are 1  $\rightarrow$  output is 1

$$Y = A \cdot B$$

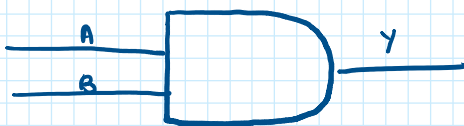


Truth Table

INPUTS		OUTPUT
A	B	Y
0	1	0
0	0	0
1	1	1
1	0	0

## OR GATE

Any input is 1  $\rightarrow$  Output is 1

$$Y = A + B$$

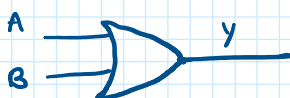


## Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

## NOT GATE

Any one input  $\rightarrow$  opposite output

$$Y = \bar{A}$$

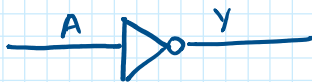


## Truth Table

INPUT	OUTPUT
A	Y
0	1
1	0
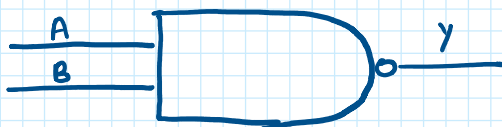
## NAND GATE

NOT (AND) = NAND.

Active low: If any input is 0  $\rightarrow$  Output is 1




## Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0
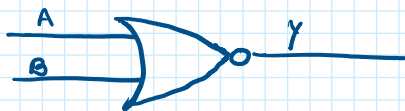
## NOR GATE

NOT (OR) = NOR

Active high: If any input is 1  $\longrightarrow$  output is 0



## Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## XOR GATE

ODD function gate: If there is an odd no. of 1s in input  $\longrightarrow$  Output is 1

## Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

MIN TERMS:  $\bar{A}B + A\bar{B}$


MAX TERMS:  $\bar{A}\bar{B} + AB$

$$Y = \bar{A}B + \bar{B}A$$

$$Y = A \oplus B$$


symbol

Symbol

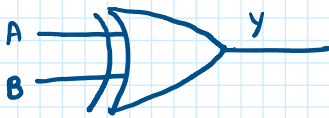

### 3- INPUT XOR GATE

INPUTS			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0
1	0	1	0
0	1	1	0
1	1	1	1

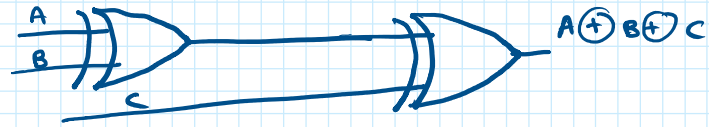

Associative law

$$(A \oplus B) \oplus C = A \oplus (B \oplus C)$$

$$\begin{aligned}
 Y &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \quad \left\{ \text{SOP form} \right. \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\
 &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\
 &= A \times + A \times \\
 &= A \oplus X \\
 &= \underline{\underline{A \oplus B \oplus C}}
 \end{aligned}$$

### PROPERTIES OF XOR GATE

- Identity element:  $A \oplus 0 = A$
- $A \oplus 1 = A'$
- $A \oplus A = 0$
- $A \oplus \bar{A} = 1$
- Commutative law:  $A \oplus B = B \oplus A$
- Associative law:  $A \oplus (B \oplus C) = (A \oplus B) \oplus C$

## XNOR Gate


not of XNOR.

EVEN function gate: Even no. of 1s  $\rightarrow$  Output is 1

Truth Table

INPUTS		OUTPUT	
A	B	Y	
0	0	1	$\bar{A}\bar{B}$
0	1	0	$\bar{A}B$
1	0	0	$A\bar{B}$
1	1	1	$AB$
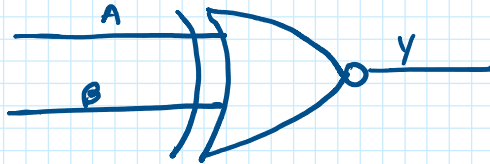
$$Y = A \cdot B + \bar{A} \cdot \bar{B}$$
$$Y = A \odot B$$



## THREE INPUT XNOR GATE

INPUTS			OUTPUT
A	B	C	Y
0	0	0	1
1	0	0	0
0	1	0	0
0	0	1	0
1	1	0	1
0	1	1	1
1	0	1	1
1	1	1	0