

## 4. Types of Diode Breakdown, Diode Approximations

13 September 2023 10:50

### TYPES OF DIODE BREAKDOWN

#### Avalanche breakdown

Under reverse bias,

Voltage increases → Depletion region widens → Accumulation of more immobile ions


Collision with ←  
other atomic  
structures

Kinetic energy ←  
is provided  
to charge carriers

Electric field  
is generated

↓  
Releases more  
charge carriers;  
covalent bonds broken,  
electron-hole generating

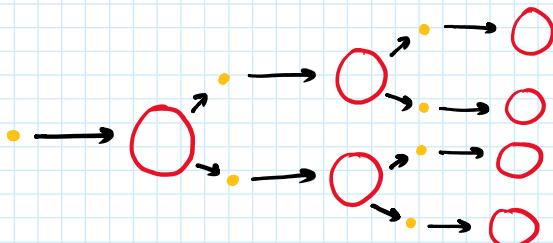- Happens due to impact ionisation / avalanche multiplication




- Motion of these charge carriers creates a sudden jump in current, often damaging the diode itself

#### Zener Breakdown

- Occurs in Zener diode → Both p and n heavily doped
- Due to more charge carriers, depletion region is narrower in normal state
- Smaller reverse bias voltage → stronger electric field

↓  
more charge carriers  
liberated

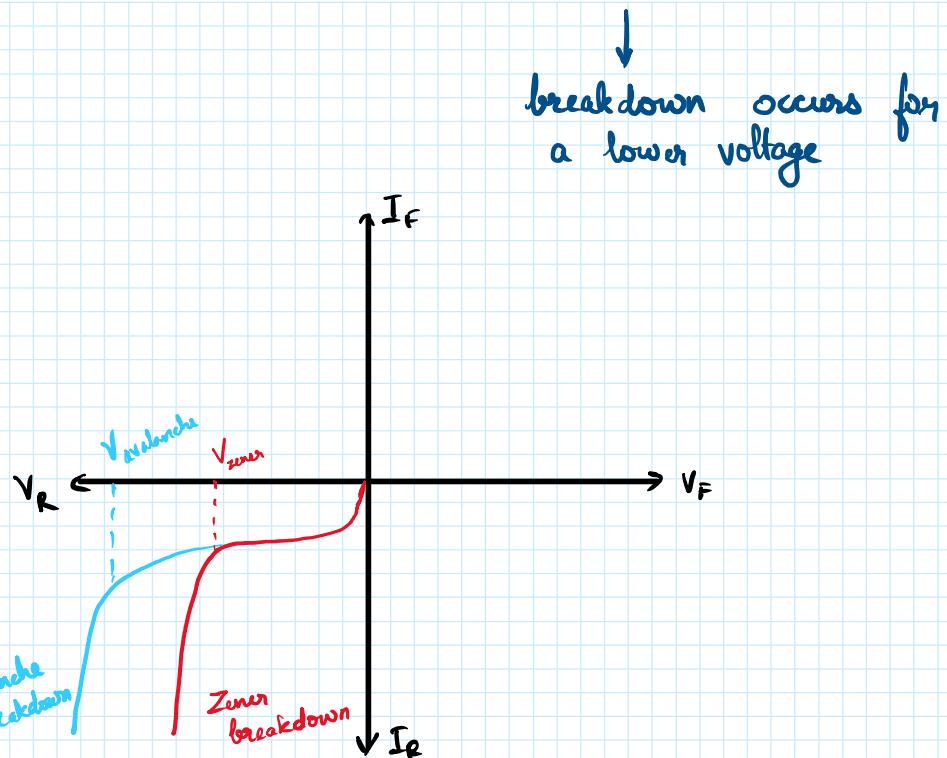

## DIODE APPROXIMATIONS / EQUIVALENT DIAGRAMS

Mathematical method to approximate non-linear behaviour of real diodes

three types

First Approximation (Ideal Diode Characteristics)

Second Approximation (Simplified Diode Characteristics)


Third Approximation (Linear Piece-wise Diode Characteristics)
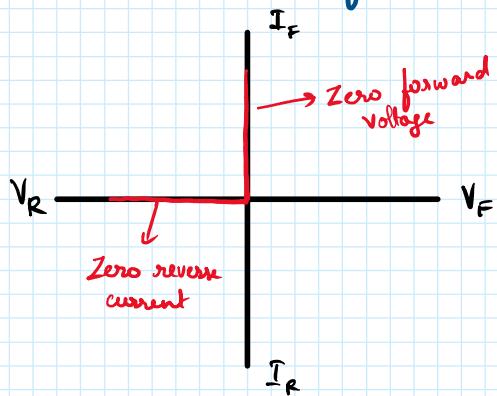
### First Approximation (Ideal Diode Characteristics)

**FORWARD BIAS:** Closed switch, no voltage drop




**REVERSE BIAS:** Open switch, infinite resistance



### Second Approximation (Simplified Diode Characteristics)

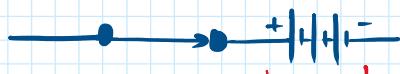
## Second Approximation (Simplified Diode Characteristics)

**FORWARD BIAS:** In series with a battery to turn on, specific knee voltage is given



→ 0.7 V or greater for Si

**REVERSE BIAS:** Open switch

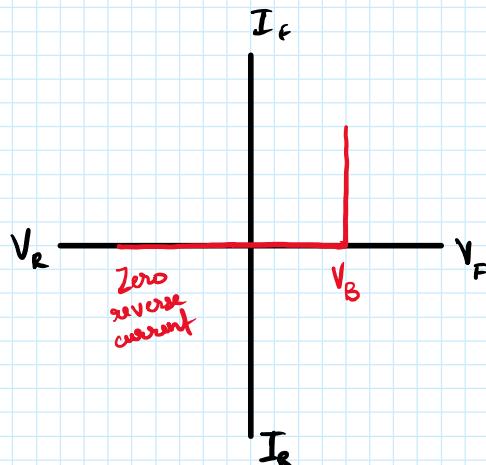


## Third Approximation (Linear Piece-wise Diode Characteristics)

**FORWARD:** Includes knee voltage as well as voltage across bulk resistance  $R_B$


Voltage drop  $V_D$

$$V_D = 0.7 \text{ V} + (I_D)(R_B)$$

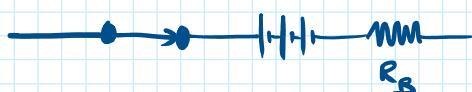Annotations: "knee voltage" points to 0.7 V, "bulk resistance" points to  $R_B$ , and "voltage across bulk resistance" points to the term  $(I_D)(R_B)$ .




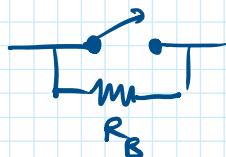**REVERSE:** Open switch with  $R_B$  in parallel




$I_f$



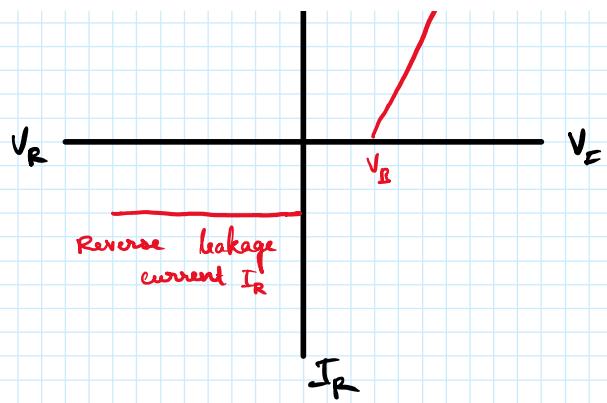

### PROBLEMS

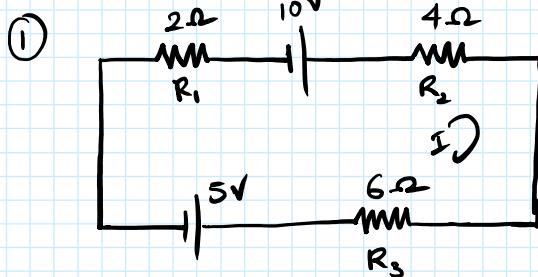

Sohu: Using KVL,

→ REVISE

$$10 - 4I - 6I - 5 - 2I = 0$$



$$5 - 12I$$


② A Si diode and Ge diode are connected in series with a  $2k\Omega$  resistor. If each diode has an internal resistance of  $5\Omega$ , find the diode current for both piece-wise linear circuit and simplified circuit if applied voltage is

(a)  $V_D = 1V$

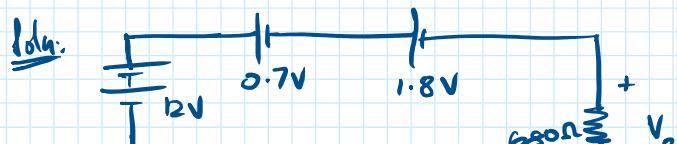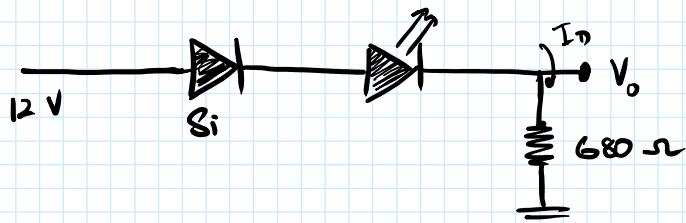(b)  $V = 5V$

③ Determine  $V_o$ ,  $I_D$  for given series diode circuit. Assume LED voltage as  $1.8V$



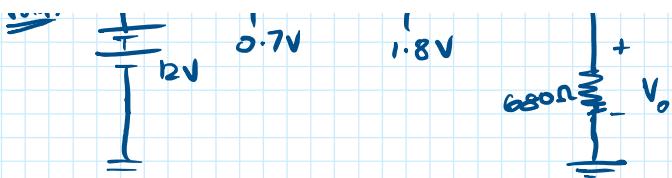



$$V_o = 12 - 0.7 - 1.8 \\ = \underline{\underline{9.5 \text{ V}}}$$

$$9.5 - 680 I_D = 0$$

$$I_D = \frac{-9.5}{-680}$$

$$= \underline{\underline{0.013 \text{ A}}}$$

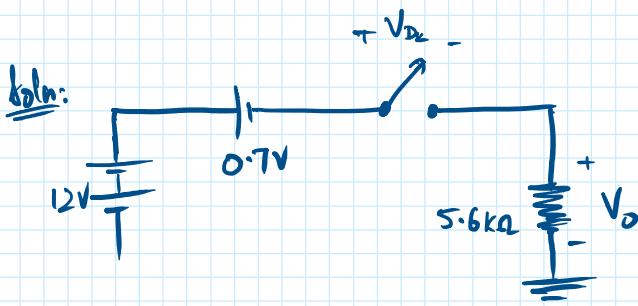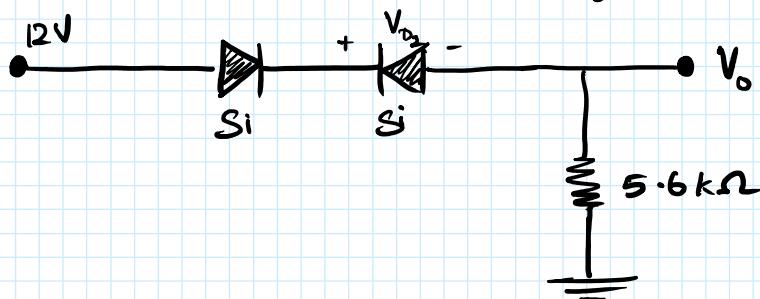④ Determine  $I_D$ ,  $V_{D_2}$  &  $V_o$  for given circuit




$$I_D = 0$$



$$V_o = 5.6 \text{ k}\Omega \times I_D$$

$$V_o = 0$$

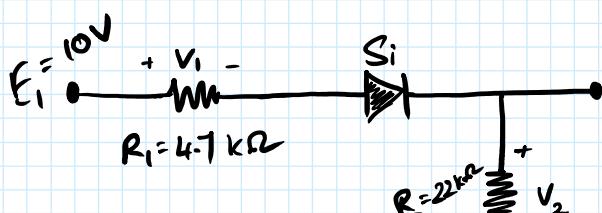⑤ Determine  $V_1$ ,  $V_2$ ,  $V_o$ ,  $I$  in the given circuit



$$R_1 = 4.7 \text{ k}\Omega$$

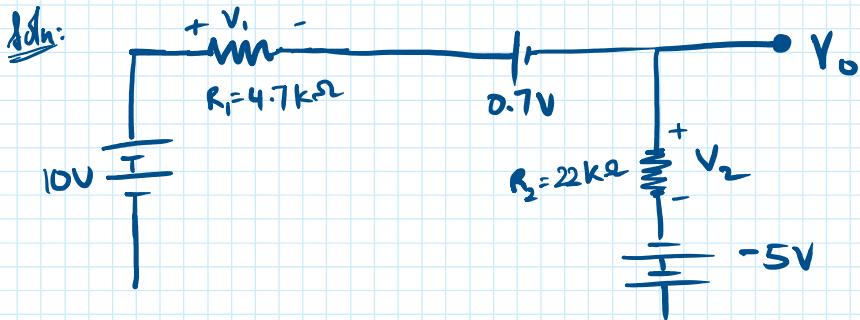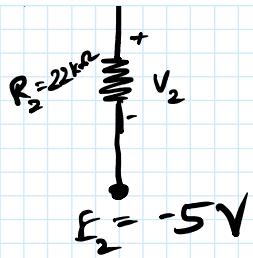

Using KVL,

$$10 - 4.7kI - 0.7 - 22kI + 5 = 0$$

$$14.3 - 26.7kI = 0$$

$$I = \frac{-14.3}{-26.7 \times 10^3} = 5.35 \times 10^{-4} \text{ A}$$

$$V_1 = IR_1$$

$$= 5.35 \times 10^{-4} \times 4.7 \times 10^3$$


$$= 2.51V$$


$$V_2 = IR_2$$

$$= 5.35 \times 10^{-4} \times 22 \times 10^3$$

$$= 11.77V$$

$$-5 + V_2 - V_0 = 0$$

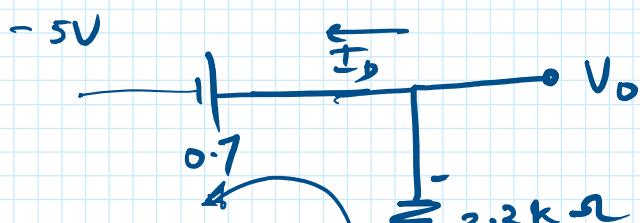

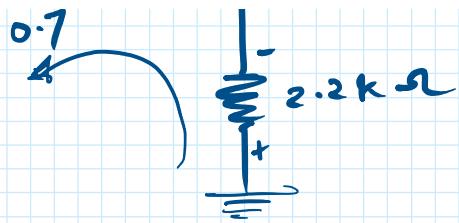

$$-2.2kI - 0.7 + 5 = 0$$

$$I = \frac{-4.3}{-2.2 \times 10^3} = 1.95 \times 10^3 A$$

~~A~~

$$V_o = I(2.2k)$$

$$= \underline{\underline{4.3 V}}$$